

Ease of build	Advanced
-partscount	High
-density	High
Parts sourcing	Normal
Enclosure fitting	Normal
Debugging level	Advanced

HiFi Headphone Amp 2021

+ Stereo Simulation

OVERVIEW

If you wish to listen to your guitar via headphones in high quality – this circuit is for you!


It also is designed to be used for recording purposes. You might need a speaker cabinet simulator in front to color your signal and eliminate unwanted distortion frequencies you usually do not hear when listening through a guitar amp. We do recommend the runoffgroove Condor for this.

V2021 has an optimized layout and changes all upright resistors from previous versions.

GENERAL

The headphone amp is a HiFi design utilizing a special chip for that purpose. The stereo simulation is basically generated from a time-delayed signal generated out of the original signal using multiple allpass-type filters.

SCHEMATIC


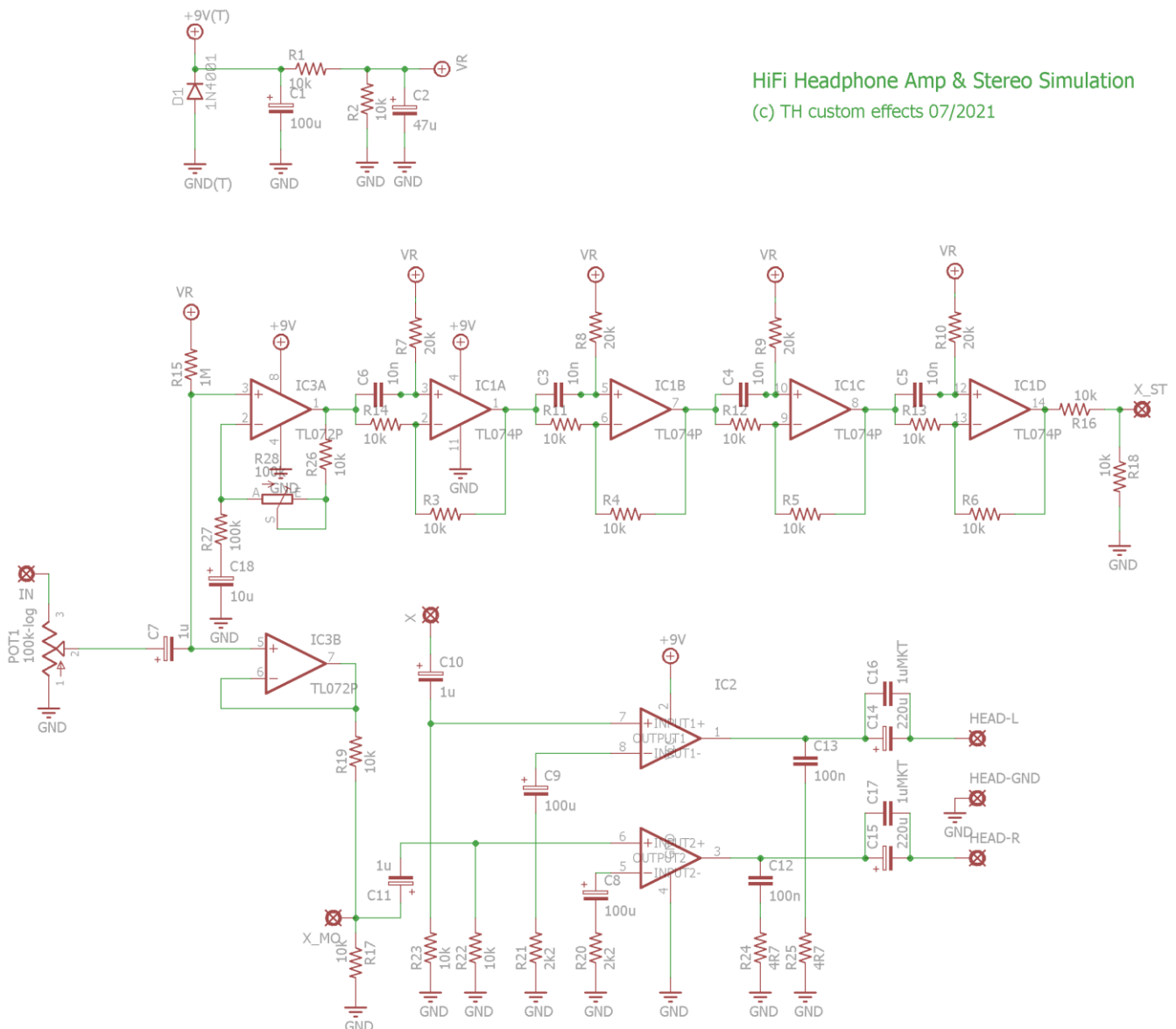



BILL OF MATERIALS

	Parts	Value	Qty	Description
Resistors	R1-R6,R11-R14,R16-R19,R22,R23,R26	10k	17	
	R7,R8,R9,R10	20k*	4	Use 220k,68k,20k,11k for more selective phase shifting
	R15	1M	1	
	R20,R21	1k2-2k2	2	
	R24,R25	4R7	2	Or 5R1
	R27	100k	1	
	Capacitors	C1,C8,C9	100u	3
C2		47u	1	pol. electro
C3-C6		10n	4	box film
C7,C10,C11		1u	3	pol. electro
C12,C13		100n	2	box film
C14,C15		100u-220u	2	pol. electro
C16,C17		1u	2	box film
C18		10u	1	pol. electro
Diodes		D1	1N4001	1
Pots	R28	100k	1	6mm trim
	POL1 (VOLUME)	100k-log	1	Potentiometer
ICs	IC1	TL 074	1	
	IC2	TDA 2822M	1	
	IC3	TL 072	1	
Other	SW1	SPDT	1	

BUILDING

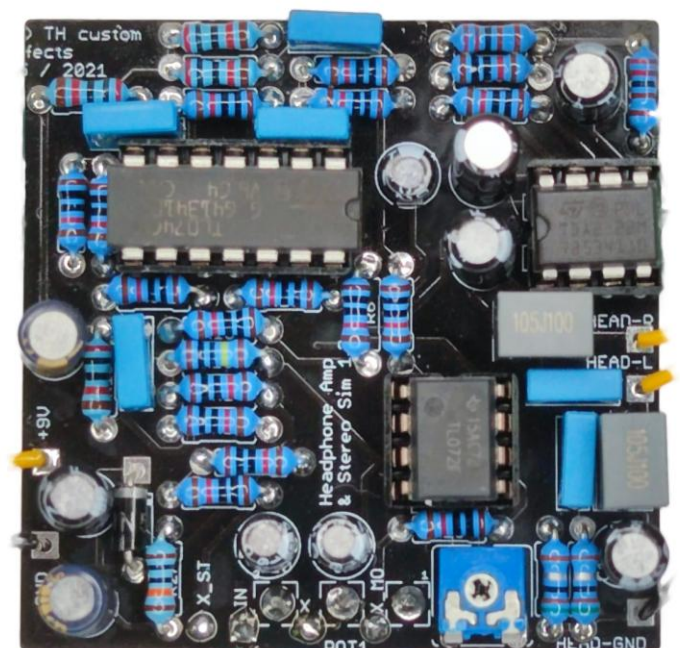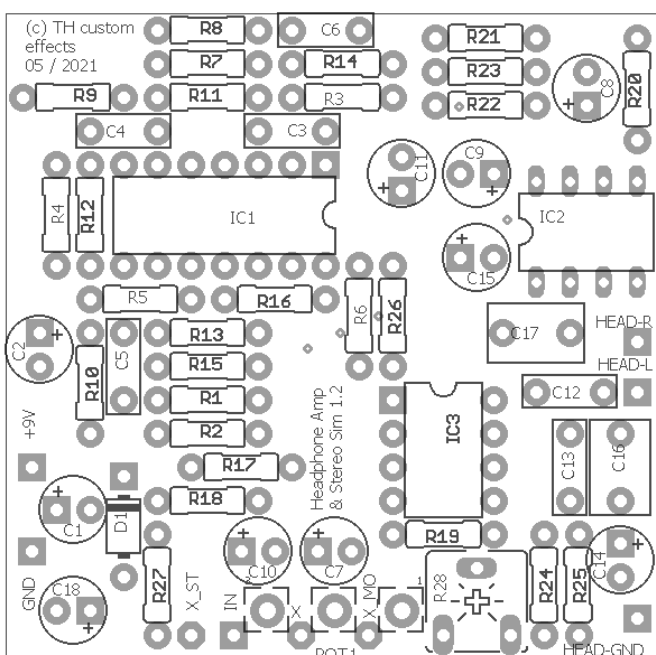
Start populating the diode and resistors first. Then IC sockets and the low height box film capacitors. Last go the electro caps and the 1uF box caps.



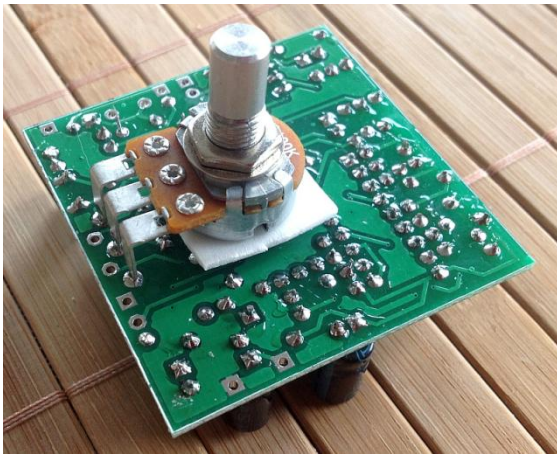

Next put the board mounted pot on the backside. Please cover the pots backside with tape so there cannot be any shortcuts with the solder pins of the populated board. Don't forget to clip off the notch.

WIRING

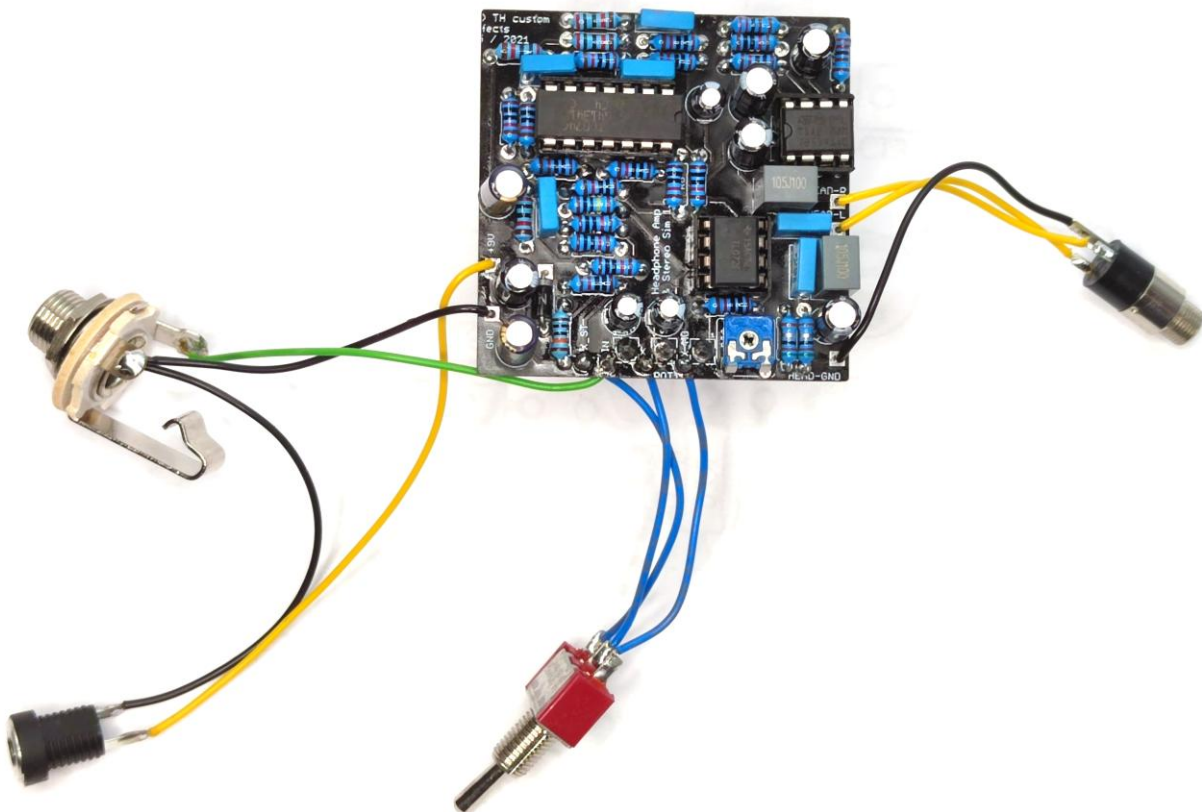

TROUBLES AND SHOOTING THEM

Since this circuit was initially released years ago we noticed sometimes people had issues with it. Sometimes people claim the TDA2822 gets hot.

There are various reasons but interestingly they are not because of a faulty TDA 2822.

The overall amplification is set by R21 and R20. You might want to raise the resistors value to reduce the overall gain of the amplifier.

In other cases replacing the TL072 fixed this! We don't know why exactly this happens but often replacing the TL072CN with TL072IP fixed the issue.

FINALLY

This is how it can look when boxed up.



DISCLAIMER & LICENSE

PCBs purchased from TH custom effects are intended for DIY / non-commercial use only. It is not allowed to redistribute the PCBs and artwork from this document. However, you can use these instructions and PCBs to build and sell your own product based on PCBs ordered from TH custom effects.