

# AZABACHE V1.1

Runoffgroove's overdrive inspired by classic Fender amps

## OVERVIEW


All credit for the circuit goes to <http://runoffgroove.com>. You will also find a lot of [sound samples](#) and [documentation](#) on their website.

## GENERAL

This is my attempt on an easy-to-use PCB for this great circuit. According to runoffgroove this is their special approach to a Fender-like overdrive. I did built it and it really sounds like it.

Revision 1.1 optimizes the layout to make the board smaller. Testpoints will make the biasing of the JFETs easier.

## SCHEMATIC



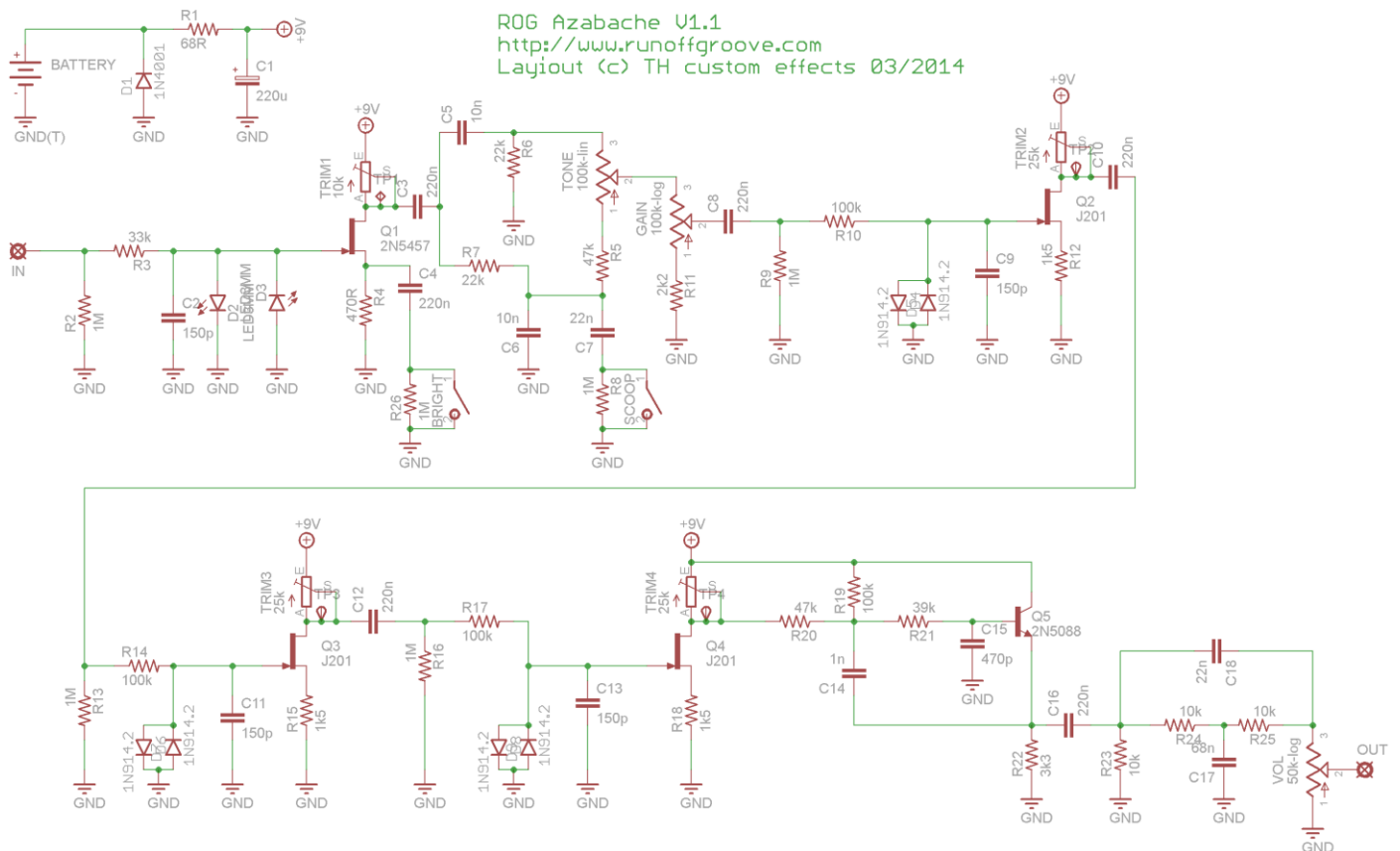


## BILL OF MATERIALS

	<i>Device#</i>	<i>Qty</i>	<i>Value</i>	<i>Comment</i>	
<b>Resistors</b>	R1	1	68R		
	R2,R8,R9,R13,R16, R26	6	1M		
	R3	1	33k		
	R4	1	470R		
	R6,R7	2	22k		
	R5,R20	2	47k		
	R10,R14,R17,R19	4	100k		
	R11	1	2k2		
	R12,R15,R18	3	1k5		
	R21	1	39k		
	R22	1	3k3		
	R23,R24,R25	3	10k		
	<b>Capacitors</b>	C1	1	220u	polarized elektro
		C2,C9,C11,C13	4	150p	ceram
		C3,C4,C8,C10,C12, C16	6	220n	box film
C5,C6		2	10n	box film	
C14		1	1n	box film	
C15		1	470p	ceram	
C17		1	68n	box film	
C7,C18		1	22n	box film	
<b>Diodes</b>		D1	1	1N4001	
	D2,D3	2	LED 3mm red		
	D4,D5,D6,D7,D8,D9	6	1N4148		
	<b>Transistors</b>	Q1	1	2N5457	
Q2-Q4		3	J201		
Q5		1	2N5088		
<b>Trimmer</b>		TRIM1	1	25k	6mm
	TRIM2-4	3	50k	6mm	
<b>Pots</b>	GAIN	1	100k-log	16mm right-angle print	
	TONE	1	100k-lin	16mm right-angle print	
	VOL	1	50k-log	16mm right-angle print	
<b>Other</b>	SW1,2	2	SPST		
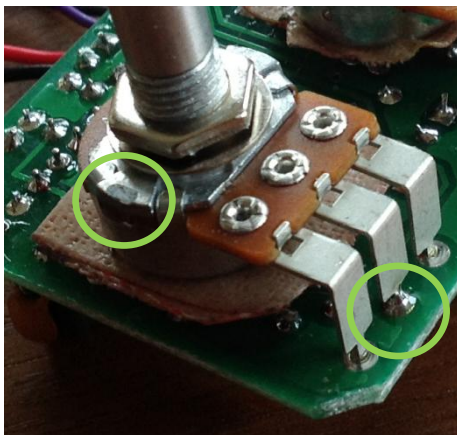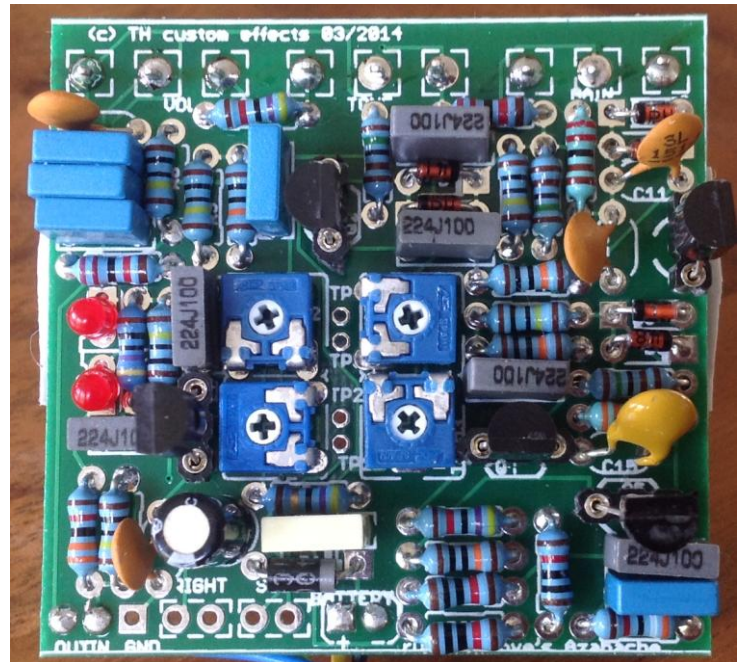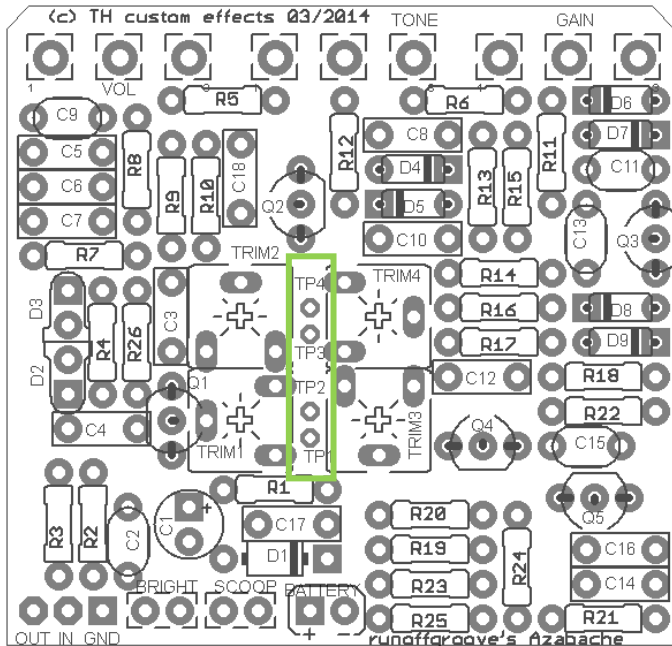
## BUILDING

Start populating the diodes and resistors first. You want to socket the transistors. Put the socket in next. Then go the trimmots. Last are the LEDs, ceramic and film box capacitors, then the electrolytic.



The board mounted pots need to go onto the other side of the board. Use some (double-sided) tape to make sure the pot cases do not shorten any pins that come through the board. As you solder them it is good practice to apply some solder to the middle pin first, then pull it back or approx. 1mm and let it harden. Then solder the other pins. This will align the pot horizontally in a better way and avoid shortcuts of the wide pot pins and the board.

Don't forget to clip of the small bracket before you mount the circuit.

## BIASING:

As there are four transistors you will have difficulty adjusting this by ear. Please use a multimeter and check that the transistor drain voltage is close to 6V for the 2N5457 (Q1) and 5V for the J201s (Q2-Q4).


To do this connect your multimeter to ground and tip the testpoints TP1-TP4 to measure the voltage. Adjust it using the corresponding trimmers TRIM1-TRIM4.

At least this should put them into their working area. You can fine-tune the transistors once you have powered the circuit up by ear.
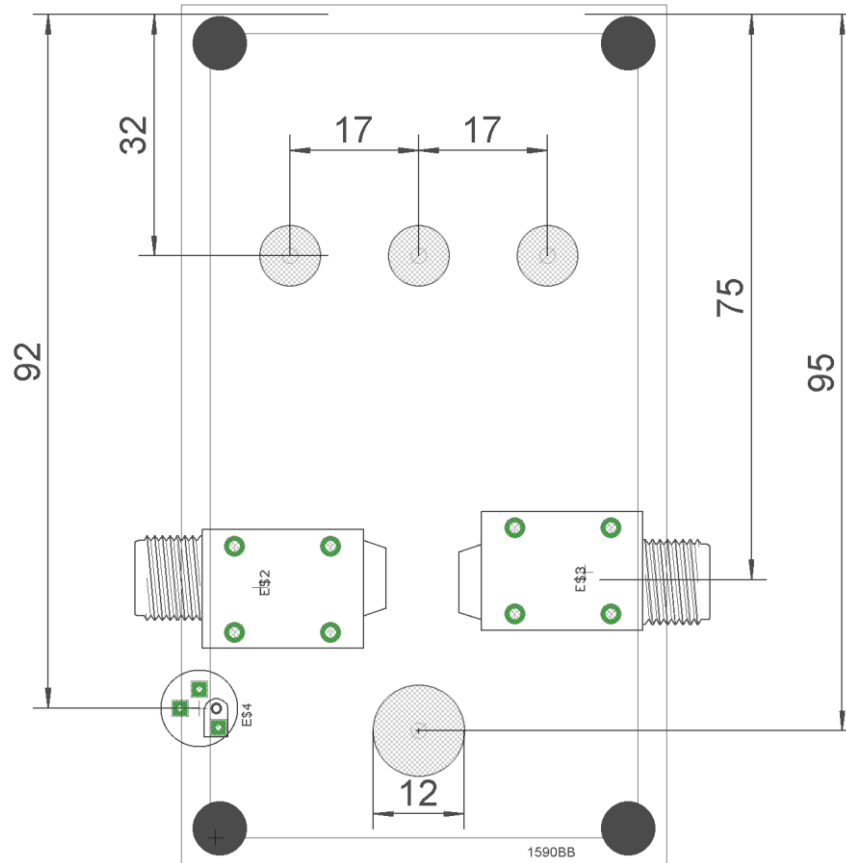
## ENCLOSURE

Drilling a 1590B enclosure (measurements in mm)

Check your printout for correct measurements before drilling!



## FINALLY

Once you managed biasing this circuit you have all the Fender-like tones available. Have fun!

## DISCLAIMER & LICENSE

PCBs based on runoffgroove circuits purchased from TH custom effects are intended for DIY / non-commercial use only. Any commercial use whatsoever is forbidden. Please contact runoffgroove for further information.